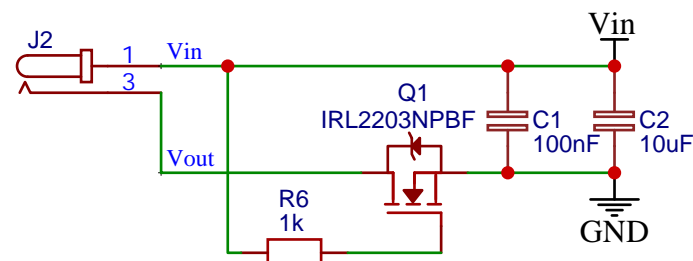



Vin is connected to LED strip, thus check if your LED strip is 5 or 12V
 WS2812B = 5V
 WS2815 = 12V



C1 and C2
 filter Vcc so when a crappy adapter is used
 and the LED switches they wont blink
 Can be adjusted if LEDs still blink;
 I prefer 1 high and 1 low filter

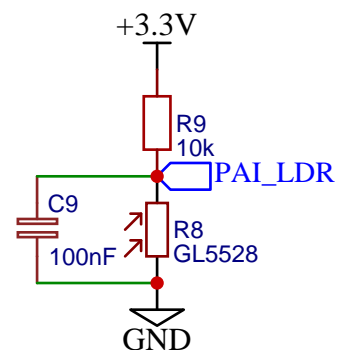Q1 Is reverse voltage protection
 Short Vout+GND and remove R6 to overtule


This part is to sense room lighting conditions



C3 helps with sudden drops between readings,
 when the LED blink (full/low power)
 the POTs seemed unstable otherwise


C4-C7 makes reading more stable
 (OEM suggestion)

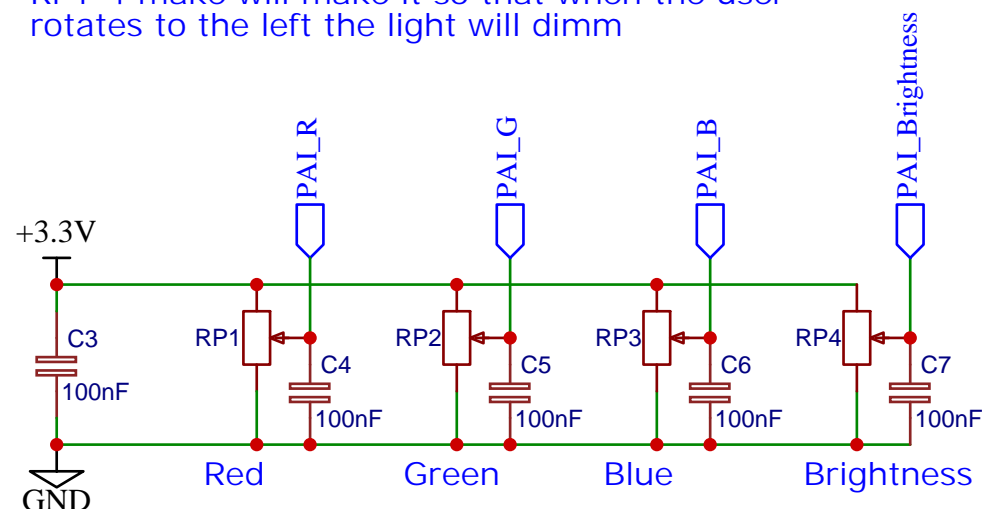RP1-4 make will make it so that when the user
 rotates to the left the light will dimm




only ADC1 works with WIFI on,
 so we need to use pins 32 to 39 for analog
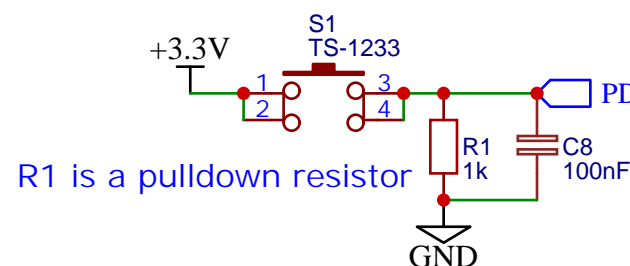
```
const byte PAO_LED = 25;
const byte PAI_R = 32;
const byte PAI_G = 33;
const byte PAI_B = 34;
const byte PAI_Brightness = 35;
const byte PDI_Button = 26;
```




R1 is a pulldown resistor

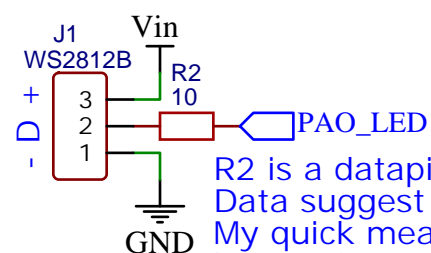

R2 is a datapin resistor for impedance matching
 Data suggest between 10 and 330ohms
 My quick measurements tell me that 220 is fine,
 but 10ohm with such sort cable is better

Chanelog:
 V1 2020-06-26 init
 V1.1 2020-07-13 Made more stable, added reverse protection and LDR
 V1.2 2020-07-15 Reversed potmeters pinout to make left low

J3, J4, J5
 are optional/reserved

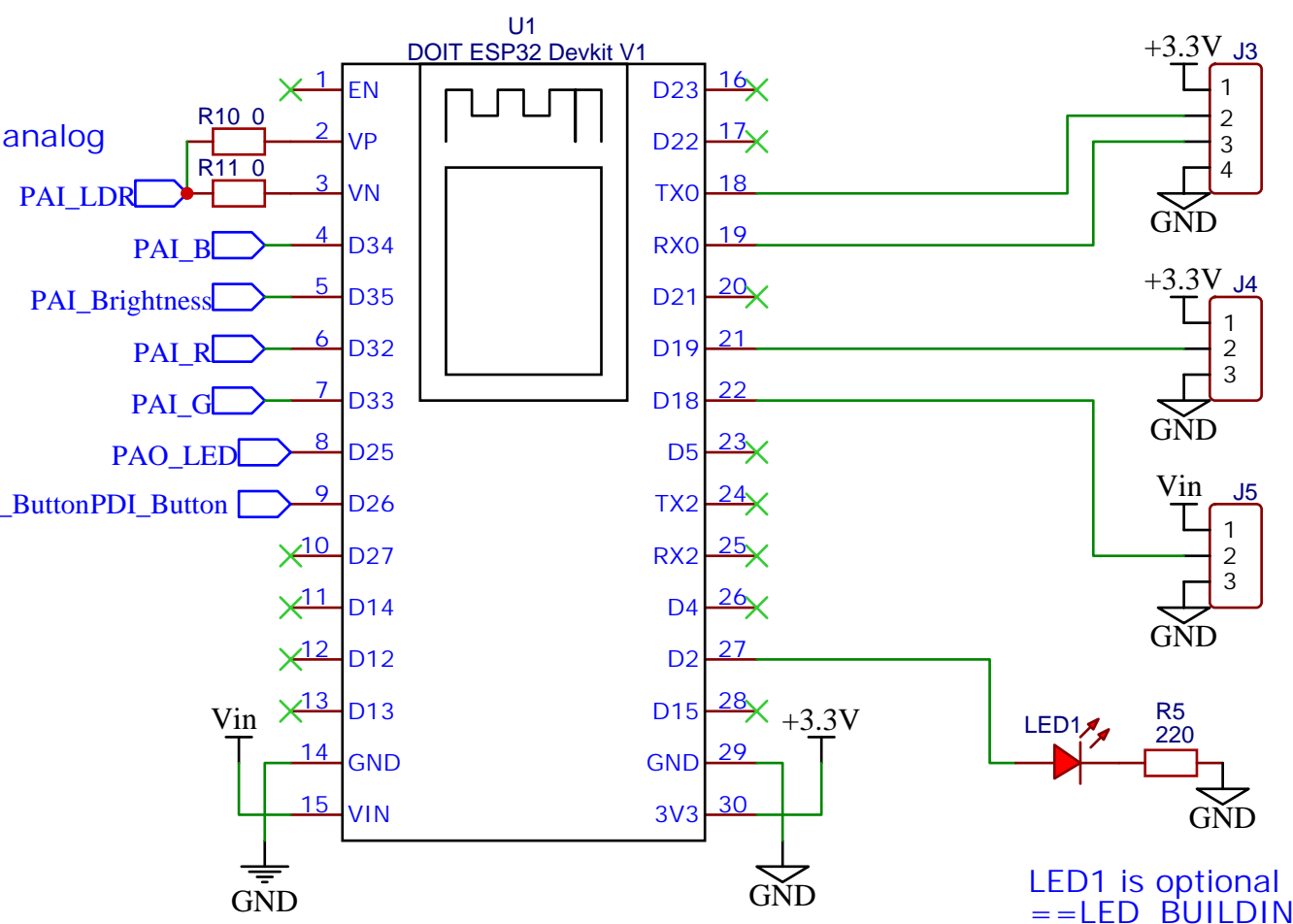

LED1 is optional
 ==LED_BUILDIN

TITLE: Schematic		REV: 1.1
EasyEDA	Company: Your Company	Sheet: 1/1
	Date: 2020-07-13	Drawn By: Jellewho